

**Uppgift 1.** a) Symmetriska laster ger  $\bar{I}_{L1} = \bar{I}_{L2} = \bar{I}_{L2}$ , med  $\bar{U}_i$  som referens.

$$P_{Last1} = \frac{P_{avg}}{\eta} = \frac{40}{0.9} = 44.4kW$$

$$P_{Last2} = 30kW$$

$$Q_{Last1} = \frac{P_{Last1} \sin \varphi_1}{\cos \varphi_1} = 33.3kVar$$

$$Q_{Last2} = \frac{P_{Last2} \sin \varphi_2}{\cos \varphi_2} = 9.9kVar$$

$$S_{tot} = \sqrt{P_{tot}^2 + Q_{tot}^2} = 86.1kVA$$

$$I_{L1} = \frac{S_{tot}}{U_H \sqrt{3}} = 124A$$

$$\cos \varphi_{tot} = \frac{P_{tot}}{S_{tot}} = 0.86$$

Vilket alltså ger  $I_{Li} = 124e^{-j30.2^\circ} A$  med  $U_i$  som referens.

b)

c) Y-kopplad last drar trev ggr mindre effekt.

$$P_{Last2,Y} = \frac{P_{Last2}}{3} = 10kW$$

$$Q_{Last2,Y} = \frac{P_{Last2,Y} \sin \varphi_2}{\cos \varphi_2} = 3.3kVar \implies$$

$$\implies \cos \varphi_{tot,Y} = \frac{P_{tot,Y}}{S_{tot,Y}} = \frac{44.4 + 10}{\sqrt{(44.4 + 10)^2 + (33.3 + 3.3)^2}} = 0.83$$

**Uppgift 2.** a)

$$P_1 = U_a I_a + U_m I_m$$

$$I_m = \frac{U_m}{R_m} = 1A$$

$$P_1 = 200 \cdot 9 + 220 \cdot 1 = 2020W$$

$$E = U_a - R_a I_a = 200 - 2.3 \cdot 9 = 179.3V$$

$$P_2 = E I_a = 179.3 \cdot 9 = 1613.7W$$

$$\eta = \frac{P_2}{P_1} = 0.80$$

b)

$$I_{a,II} = 0.5I_a$$

$$P_{1,II} = 200 \cdot 4.5 + 220 \cdot 1 = 1120W$$

$$E_{II} = U_a - R_a I_a = 200 - 2.3 \cdot 4.5 = 189.7V$$

$$P_{2,II} = E I_a = 189.7 \cdot 4.5 = 844.4W$$

$$\eta_{II} = \frac{P_2}{P_1} = 0.75$$

c)

$$U_{a,I} - R_a I_{a,I} - k_1 \Phi n_I = 0 \implies k_1 \Phi = \frac{200 - 2.3 \cdot 9}{1100} = 0.1629$$

$$I_{a,III} = I_{a,I} = 9A$$

$$U_{a,III} - R_a I_{a,III} - 0.1629 n_{III} = 0 \implies n_{III} = 487 \text{rpm}$$

**Uppgift 3.** a) Motorns potal är 6, och det synkrona varvtalet  $n_1 = 1000 \text{rpm}$ .

b)

$$s = \frac{n_1 - n_2}{n_1} = \frac{1000 - 950}{1000} = 0.05$$

c)

$$s_I = \frac{n_1 - n_{2,I}}{n_1} = \frac{1000 - 950}{1000} = 0.05$$

$$s_{II} = \frac{n_1 - n_{2,II}}{n_1} = \frac{1000 - 800}{1000} = 0.20$$

$$M_I = kU^2 \frac{s_I}{R_2}$$

$$M_{II} = kU^2 \frac{s_{II}}{R_2 + R_y}$$

$$M_{-I} = M_{II}$$

$$\frac{M_I}{M_{II}} = \frac{kU^2 \frac{0.05}{0.10}}{kU^2 \frac{0.20}{0.10 + R_y}} \implies$$

$$\implies 1 = \frac{0.5(0.1 + R_y)}{0.20} \implies R_y = 0.30\Omega$$

d) Exempelvis att förlusterna ökar eftersom eftersläpningen ökar.

**Uppgift 4.** c)

$$U_L = \frac{1}{T} \int_0^T u(t) dt = \frac{3}{T} \int_{\frac{x}{\omega}}^{\frac{x}{\omega} + \frac{T}{2}} 230\sqrt{2} \sin(\omega t) dt = \frac{2\pi}{\omega} \int_{\frac{x}{\omega}}^{\frac{x}{\omega} + \frac{\pi}{\omega}} 230\sqrt{2} \sin(\omega t) dt =$$

$$= \frac{230\sqrt{2}3\omega}{2\pi} \left[ -\frac{\cos(\omega t)}{\omega} \right]_{\frac{x}{\omega}}^{\frac{x}{\omega} + \frac{\pi}{\omega}} = 155.3 \left( 1 + \cos\left(\frac{2\pi}{x}\right) \right)$$

$$U_L = 100V \implies \cos\left(\frac{2\pi}{x}\right) = \frac{100 - 155.3}{155.3} \implies$$

$$\frac{2\pi}{x} = 1.93 \implies x = 3.24$$

$\frac{T}{3.24}$  motsvarar vinkeln  $\frac{360^\circ}{3.24} = 110.9^\circ$ . Tändvinkeln blir då

$$\alpha = 110.9^\circ - 30^\circ = 80.9^\circ$$